

# Philosophy of Topology and Component Selection for **Cost** and **Performance** in **Automotive Converters.**

Alexander Isurin and Alexander Cook

***“Engineering is a tool  
that a company can use  
to make profit.”***


# Main Requirements and Conditions for the automotive industry

- Reverse polarity protection
- Load Dump Over voltage from alternator
- Sources: battery and alternator
- Over voltage spikes to 800V
- Jump start stresses
- Electromagnetic Compatibility
- Life time, reliability

# Main Requirements and Conditions for the automotive industry


- **Mechanical challenges: Water resistance and vibration**
- CAN-bus communication capability
- High efficiency under light load and low consumption at idle and key off.
- Development cycle time pressures
- **Peak currents up to 2900A at 12V**
- Operational temperature -40C to +110C
- Electrical air-conditioning drive instead of belt drive
- Optional sources: Electrical grid
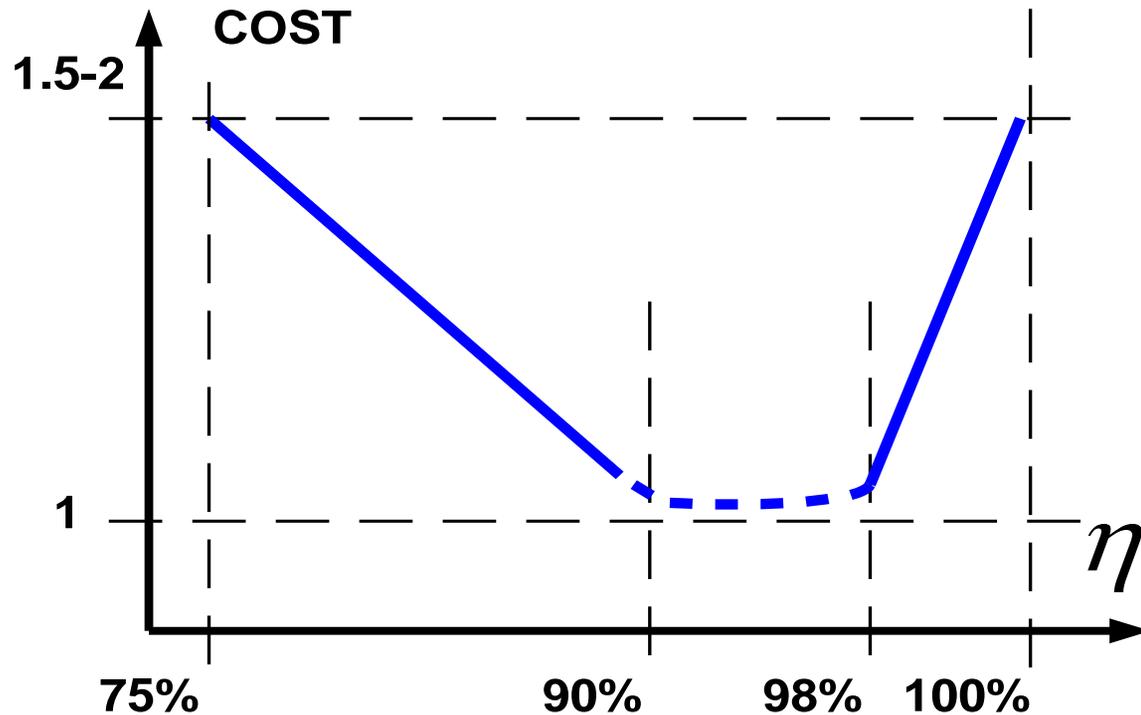
## General Relationship Between Cost and Efficiency




Cost is a strong function of efficiency as we move away from the minimum  
 $5\% \sim 8\% \Delta \text{Cost} \approx |1\% \Delta \eta|$

## Block Diagram of a Dynamic Inverter

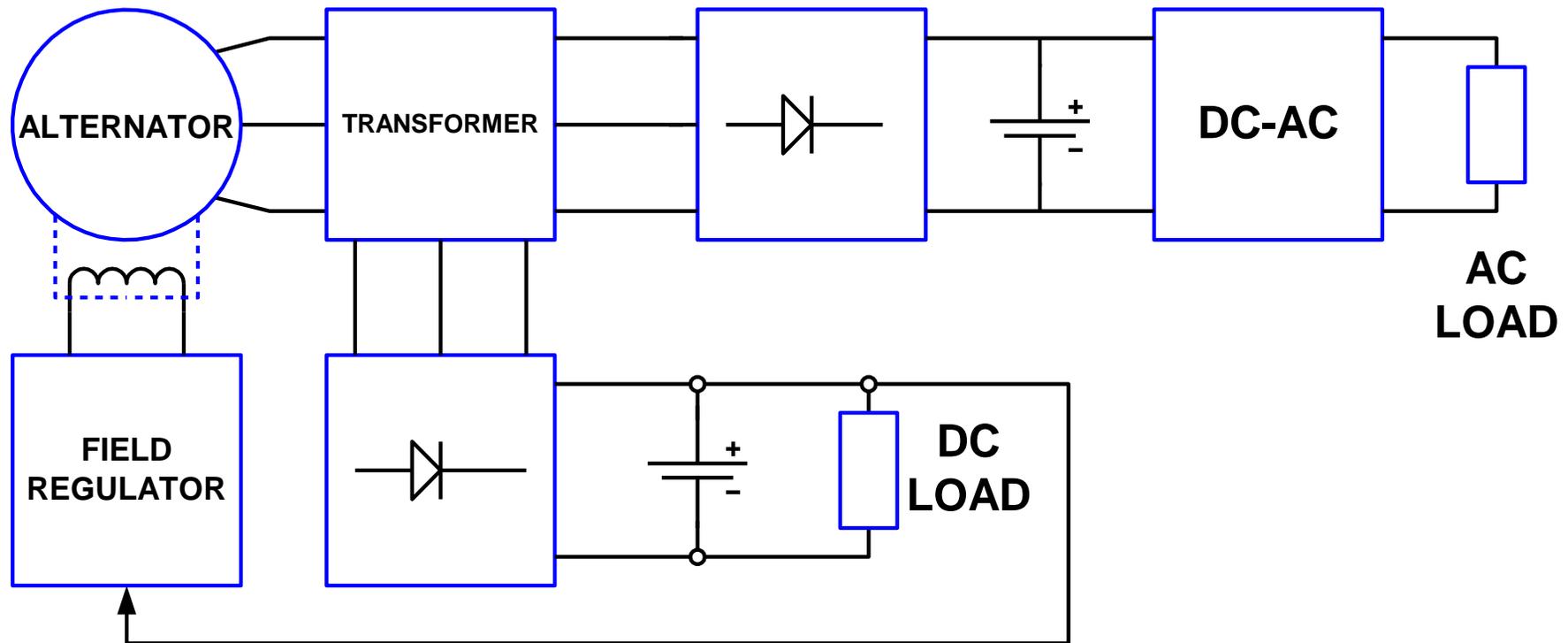
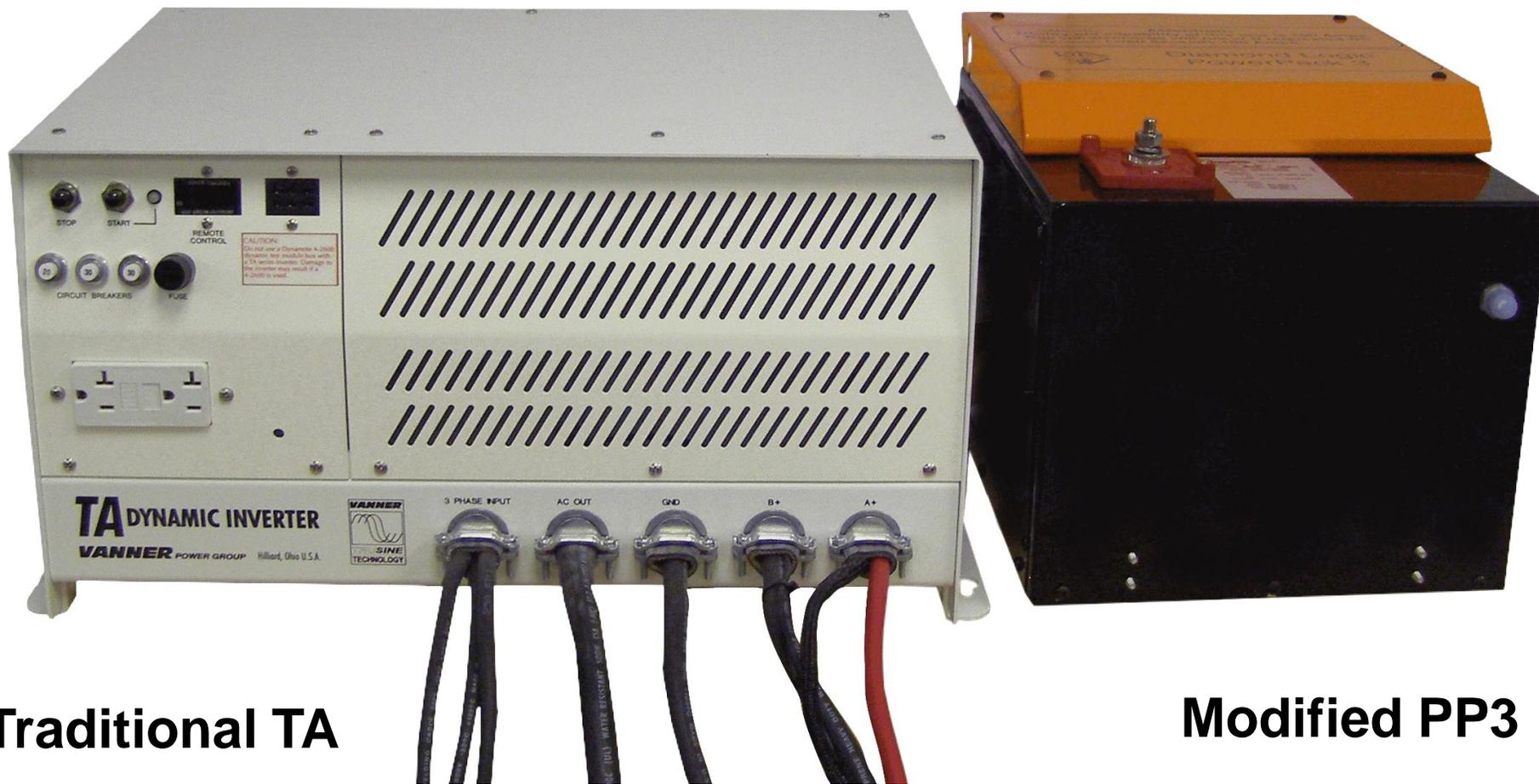
## traditional and modified dynamic inverter





**Traditional TA**

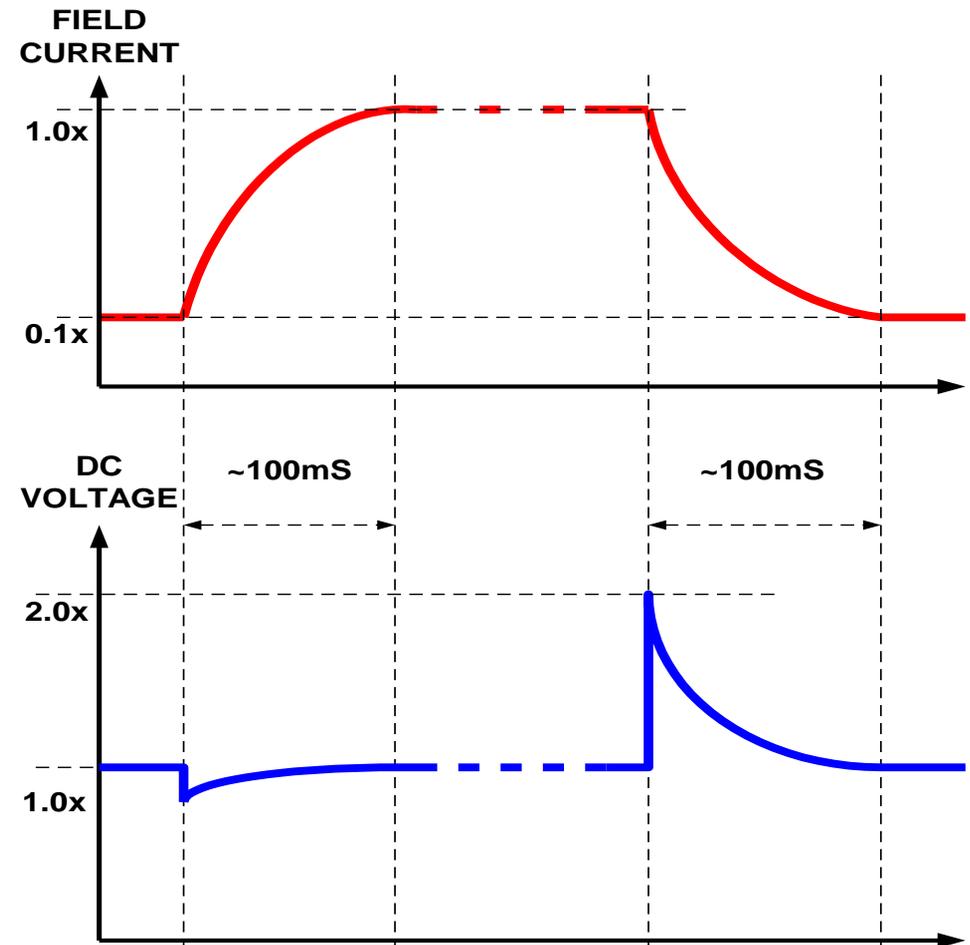
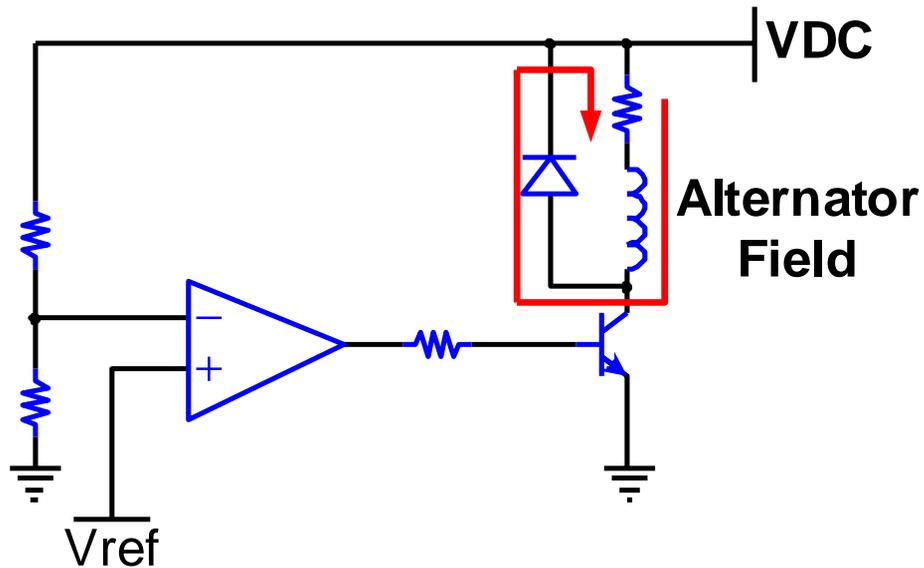
**Modified PP3**

The cost of the modified inverter  
is 17% lower relative to  
the cost of the traditional inverter

Observed in most cars and traditional inverter



## Modified Field Regulator

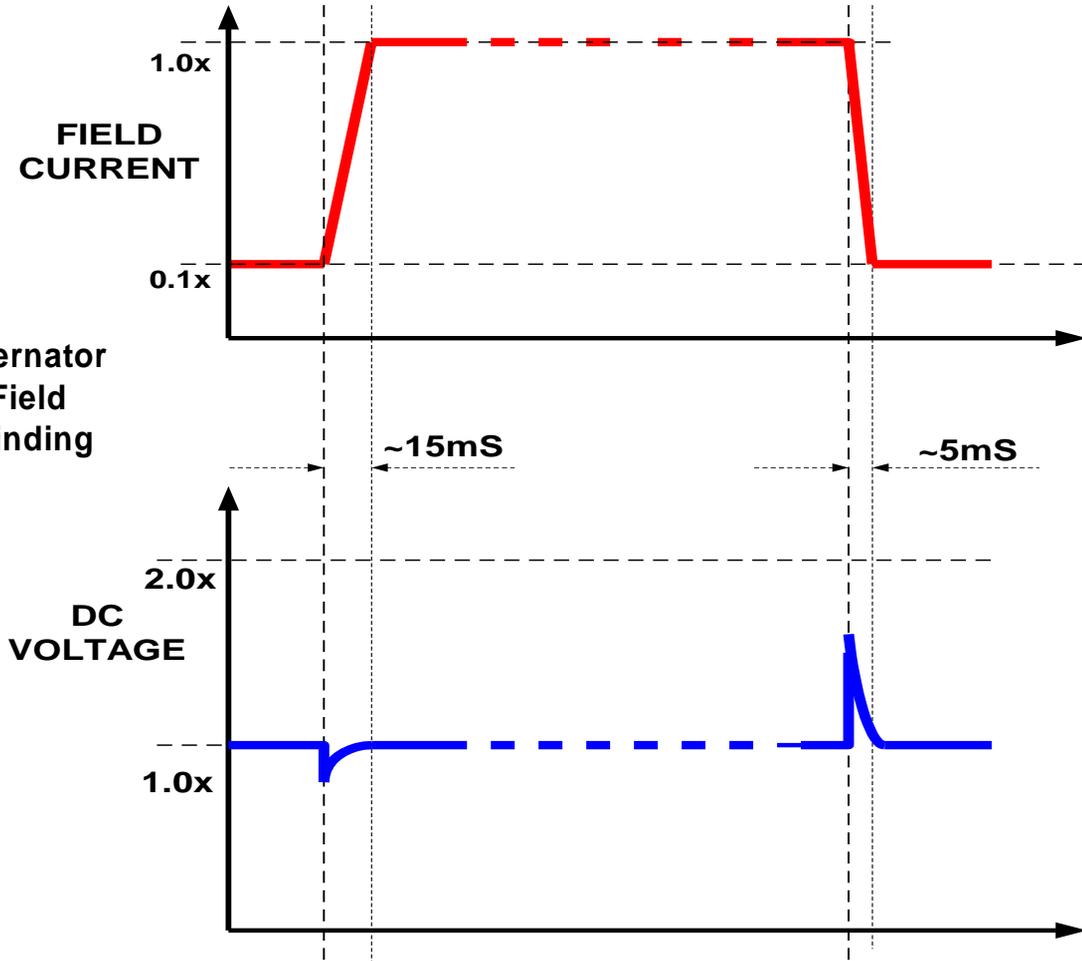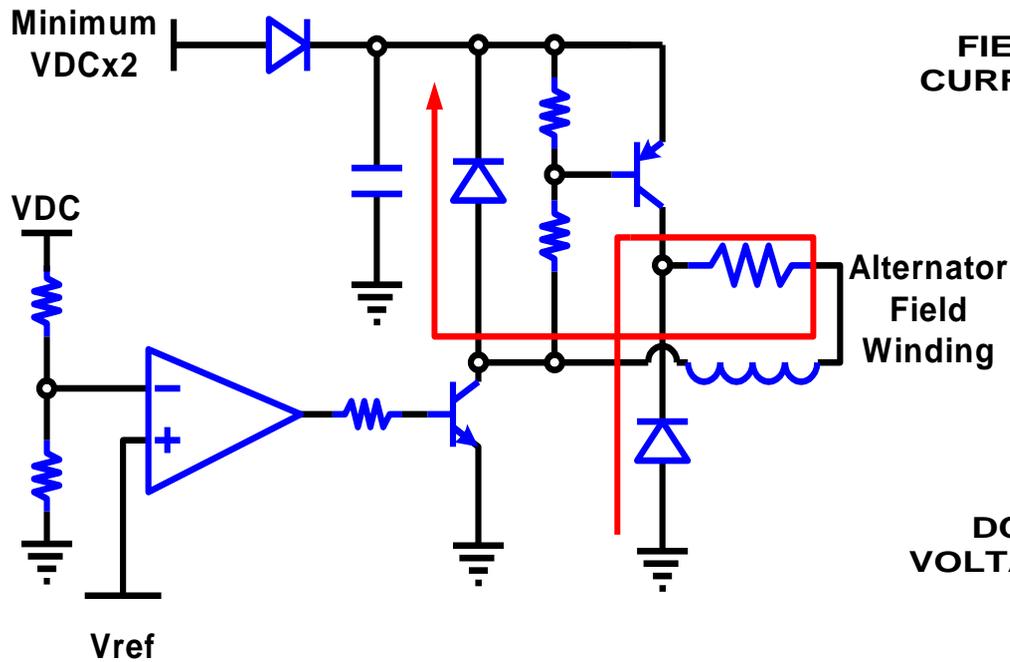


US Patent 7,106,030

2014

ISO 9001:2000 / TS-16949:2002 Registered Company

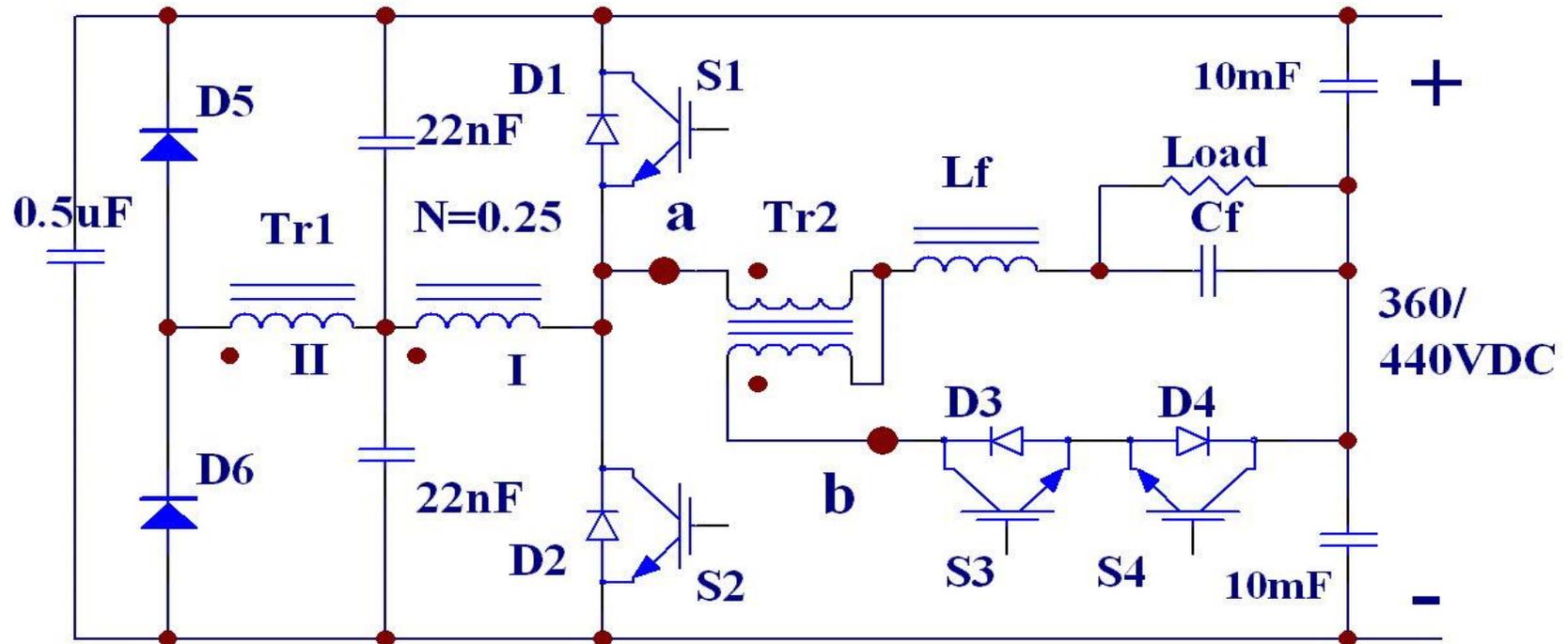
- Reduced electrical stress
- Improved response
- Reduced rating for same performance
  
- These result in reduced cost for the customer



12kW rating, efficiency ~ 97%

Presented APEC2008

## Single phase DC-AC inverter with ARCP

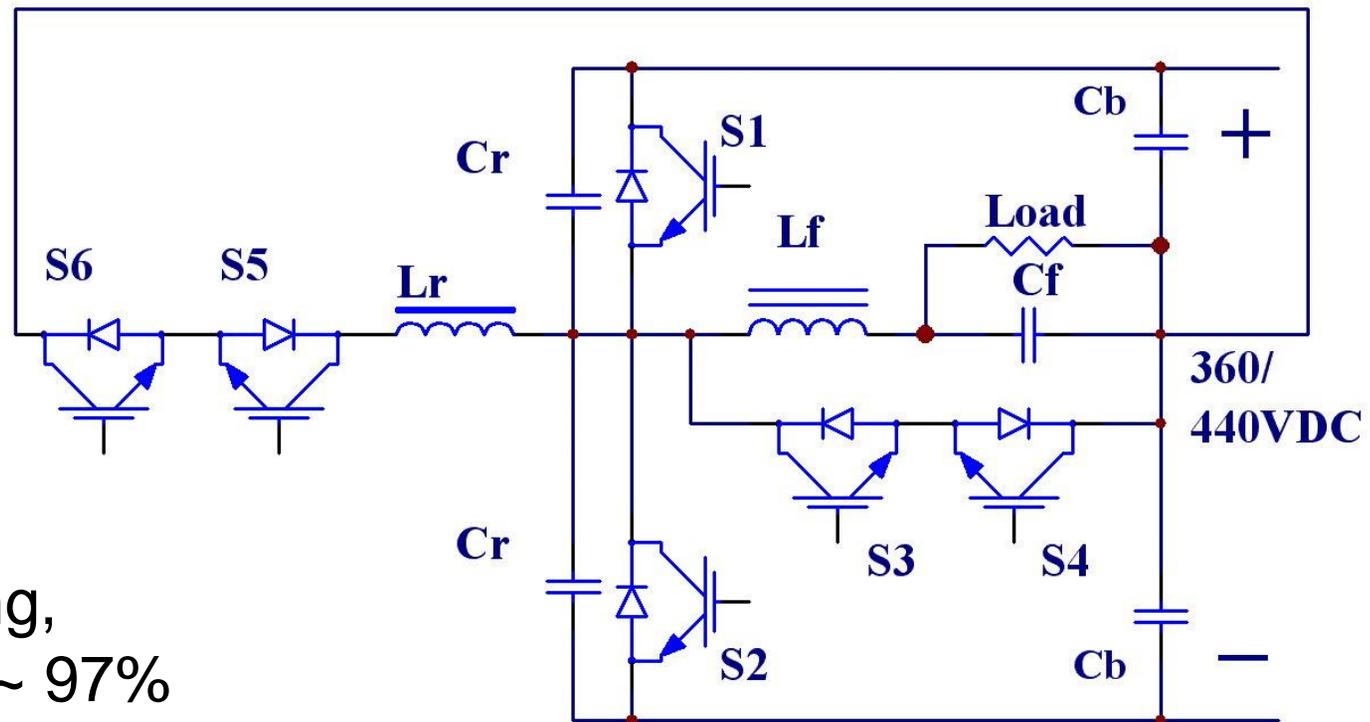

12kW rating,  
Efficiency ~ 97%



## For our Described Implementation

	Inverter with ARCP	New inverter
Cost	Add 2-3%	Basis
Efficiency	equal	equal
EMI	equal	equal
Reliability	Reduced	Basis

# Summary

- Modern components require the use of new technology and philosophies for automotive applications of power converters
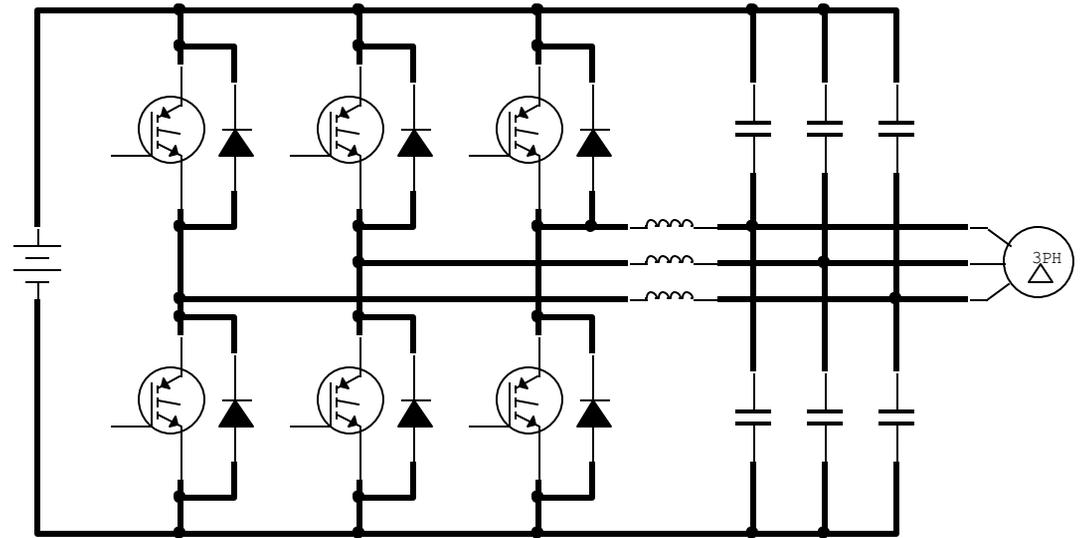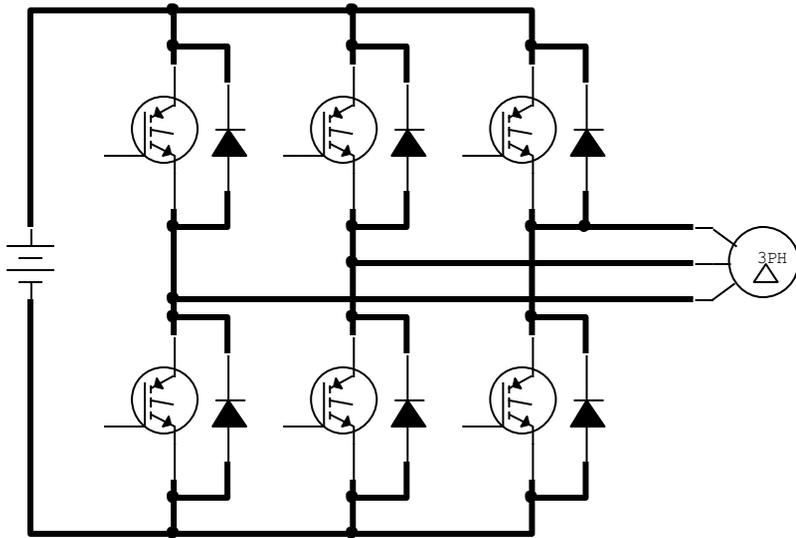
## Motor drive DC-AC Converters without and with LC Filters




**System with a filter has higher efficiency under light load,**  
**This point very important for EV vehicle.**

The converter and motor should be looked at as **one integrated power stage**. We need to see the whole picture from the start to the end. **Only this way can we get a good cost with optimal performance.**

## 9kW Bi-directional DC-DC converter

- High voltage side: 500VDC-800VDC
- Low voltage side: 20VDC-30VDC @300A
- Operational temperature: -40C to +70C @ full power
- Efficiency 94% excluding reverse polarity protection and pre-charge (93% with)
- Efficiency 84% @ 5% load
- Consumption @ idle 60W
- Life time minimum 20 years
- Cost for customer equivalent to conventional alternator

## DC-DC Converter in Step-down Mode

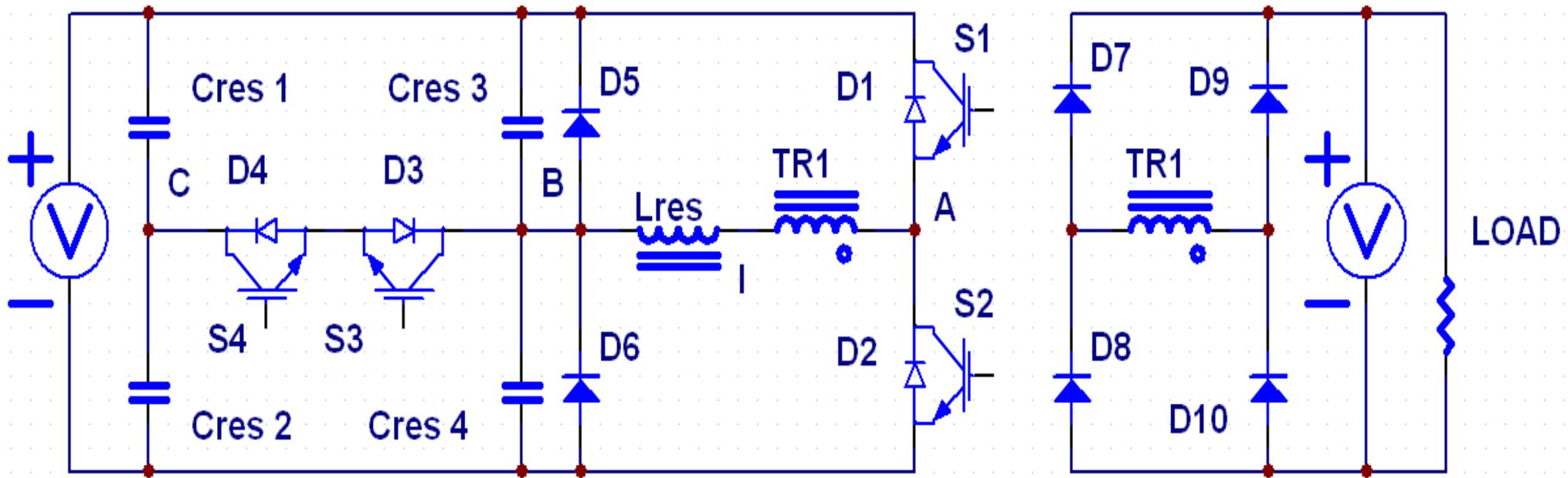


Presented APEC2006

Patent US 6,483,731

PARAMETERS	PHASE-SHIFT	NEW
Max. com. freq.	1x	2x
Load range	Limited	Unlimited
Commutation	ZVS	ZVS ZCS
Rectifier recovery	Recovery losses	Simple and soft
Paralleling of stages	Requires additional control	Simple
Transformer	Not optimal	Optimal
DC-bias	Yes	No
Control	Standard	Special
Idle losses	1.5%	0.15%
<b>COST</b>	<b>Basis</b>	<b>Basis minus &gt;10%</b>

**The both have the same performance.**
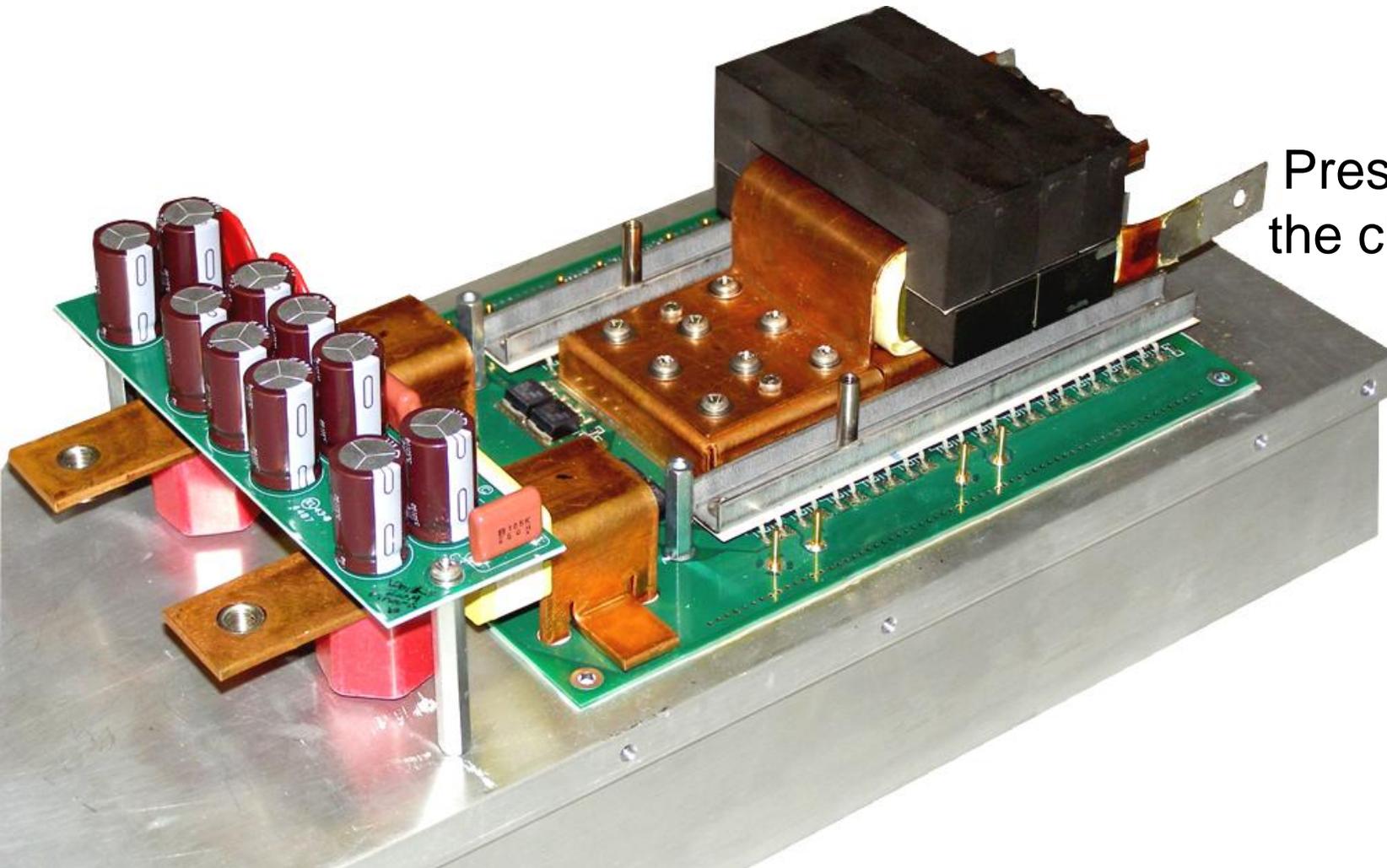
## Low voltage side power stage with integrated power transformer



Presented without  
the clamping frame

Patent US 7,123,123



## Cost and efficiency of the low-voltage side power stage with two types of transformers

Power Stage Incorporating:	Product Cost	System Efficiency
Integrated transformer	1	94%
Planar transformer	1+20%	92%

**Commutation frequency 110kHz**  
**Low voltage side rating 280A**

To use a topology where the transformer works under **optimal conditions**

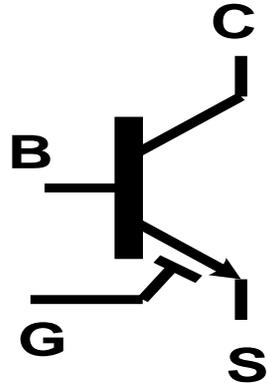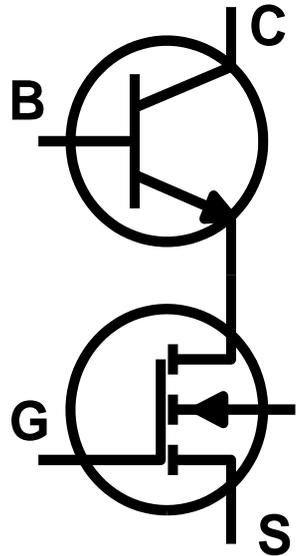The transformer itself cannot be useful alone. It can be used only as **part** of the whole power stage




**ESBT symbol and equivalent circuit, cascade connection**


## Comparison:

	ESBT total	SiC
Cost	1	3

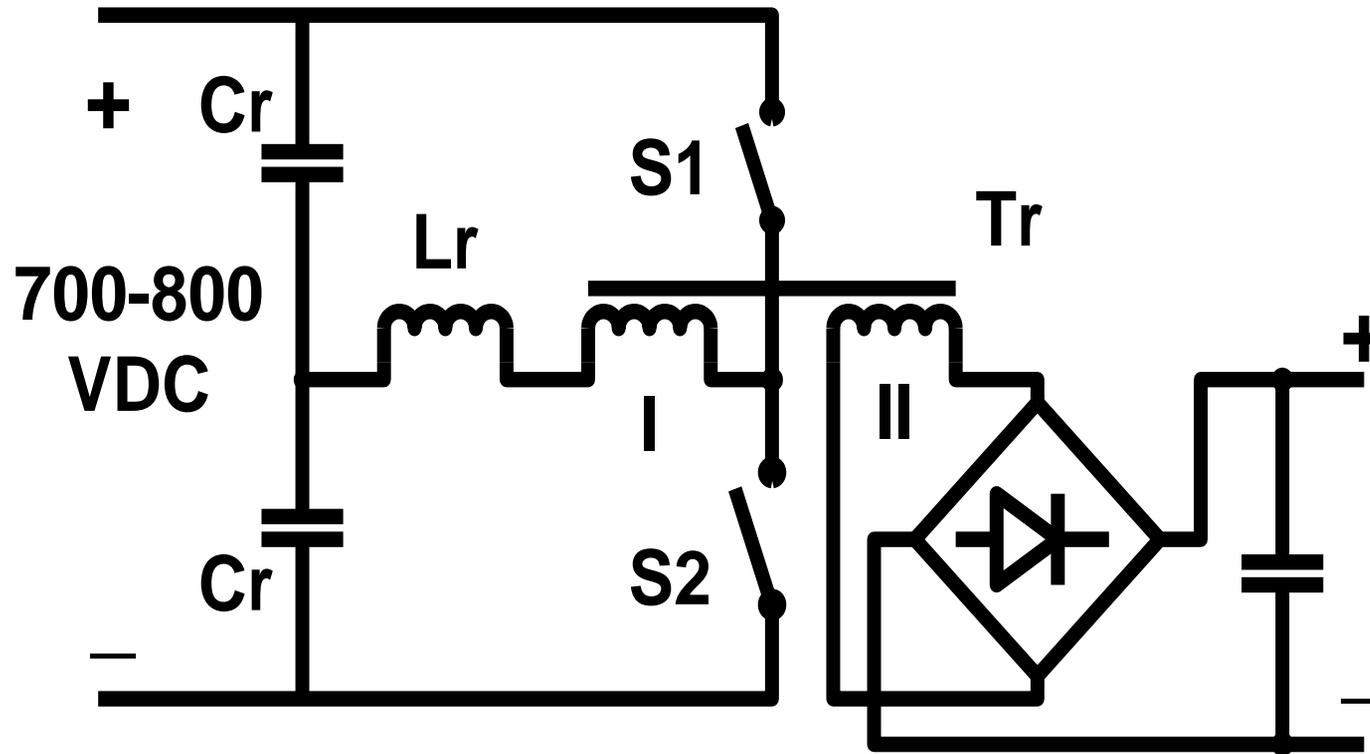
**ESBT-STE70IE120 and SiC-SAS100H12AM1**  
The both have the same performance.



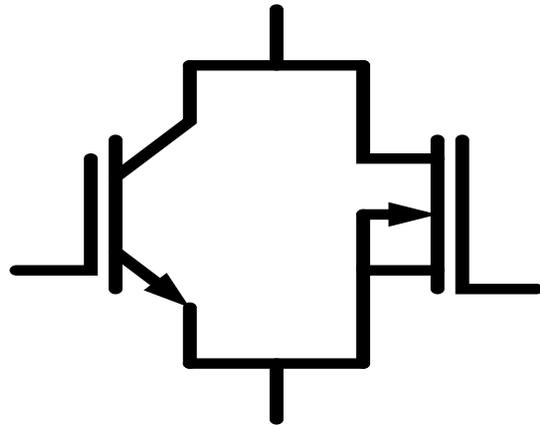**Commutation Frequency-80kHz Current via Primary winding of transformer is sinusoidal with peak 60A and duty cycle 90-95%**



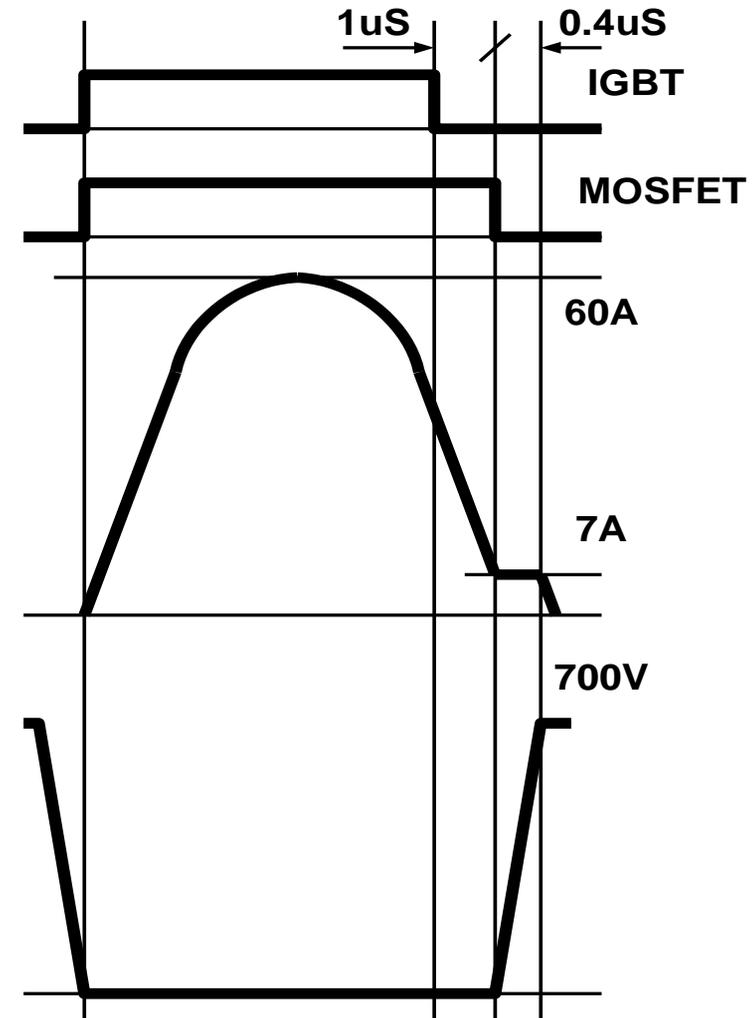**Simplified waveforms of S2 :**  
**Gate signals**  
**Current and Voltage**



## Comparison between different combinations of IGBT and MOSFETs.

**IGBT-IXEN60120    MOSFET-IXFN32N120**

	<b>IGBT</b>	<b>IGBT &amp; MOSFET</b>	<b>Two MOSFET's</b>	<b>Three MOSFET's</b>
<b>COST</b>	<b>N/A</b>	<b>1</b>	<b>1.2</b>	<b>1.9</b>
<b>Power losses per switch</b>	<b>N/A</b>	<b>109W</b>	<b>158W</b>	<b>105W</b>


**During the last 15 years the EMI requirements for electronic units for automotive applications has become more stringent, from CISPR25 class 2 to class 4. The main reason is the demand for **COMPATIBILITY.****

**The key for this point are soft-switching and maximum slew-rate 2500V/uS**
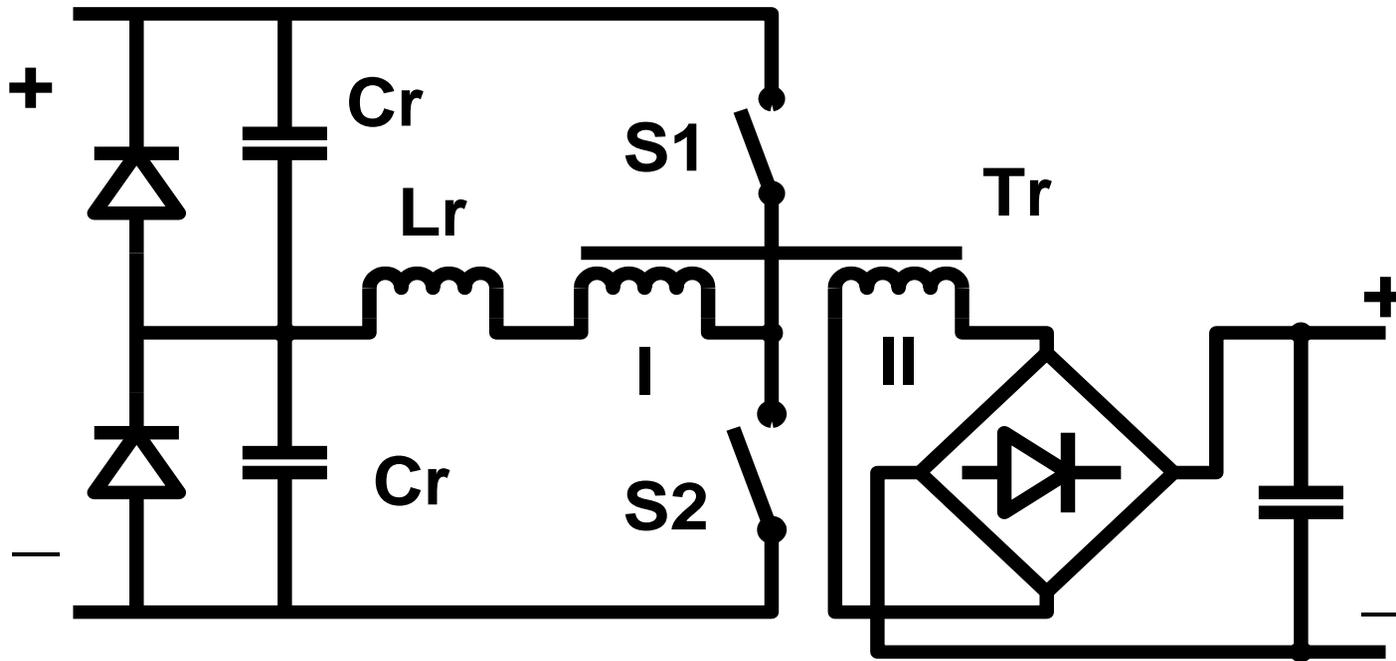
# Total cost of ownership considerations

- Product cost
- Diagnostic
- Removal and replacement cost
- Availability (stock ) cost
- Loss of use

**High cost of automotive maintenance calls  
for high reliability**



**Resonant topologies with clamp diodes provide passive power limiting.**

- Efficiency target: 92-98% The efficiency itself is not the target, rather the low cost and superior performance
  - Use soft-switch technology
  - Minimum of active components
  - Reduced quantity, and simply constructed, magnetic components
  - Use integrated magnetic components
  - Use SMA where possible
  - Use multi-level topology only when voltage is above 1000VDC
  - Limit slew rate to 2500V/uS
  - Keep operating frequency high to minimize the filter
- Maximize board mounting, minimize chassis mounting  
In other words packaging is key to realizing the benefits of the topology

**Thank You for Your  
Attention.**